

### Chapter 5, Problem 79

Determine  $v_o$  in the op amp circuit of Fig. 5.102 using *PSpice*.

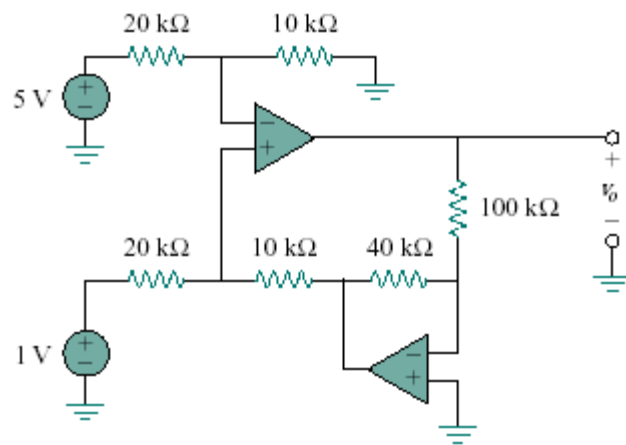


Figure 5.102  
For Prob. 5.79.