
Chapter 7, Solution 55.

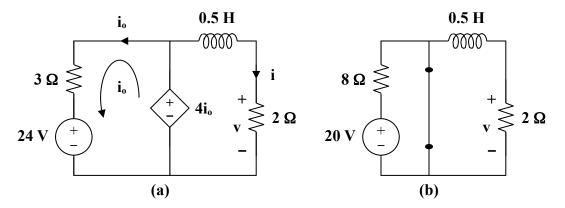For t < 0, consider the circuit shown in Fig. (a).



$$3i_{o} + 24 - 4i_{o} = 0 \longrightarrow i_{o} = 24$$

 $v(t) = 4i_{o} = 96 V$ $i = \frac{V}{2} = 48 A$

For t > 0, consider the circuit in Fig. (b).

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(0) = 48, \qquad i(\infty) = 0$$

$$i(0) = 48, \qquad i(\infty) = 0$$

$$R_{th} = 2 \Omega, \qquad \tau = \frac{L}{R_{th}} = \frac{0.5}{2} = \frac{1}{4}$$

$$i(t) = (48)e^{-4t}$$

$$v(t) = 2i(t) = 96e^{-4t} u(t)V$$