

Chapter 11, Problem 44.

Find the complex power delivered by v_s to the network in Fig. 11.69. Let $v_s = 100\cos 2000t$ V.

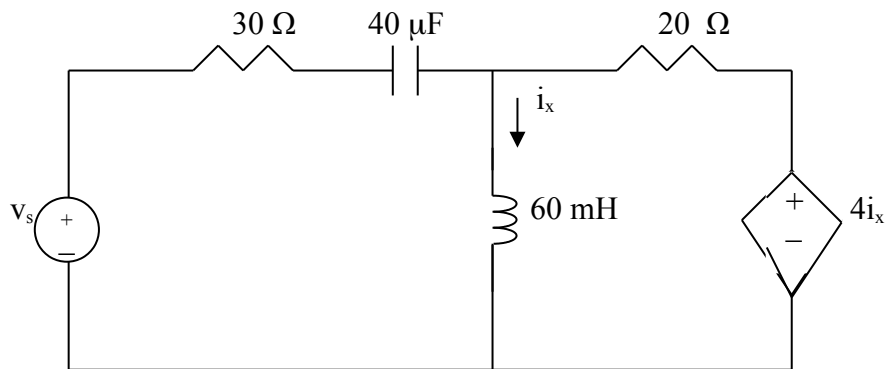


Figure 11.69
For Prob. 11.44.