

### Chapter 5, Problem 33

Refer to the op amp circuit in Fig. 5.71. Calculate  $i_x$  and the power absorbed by the 3-k $\Omega$  resistor.

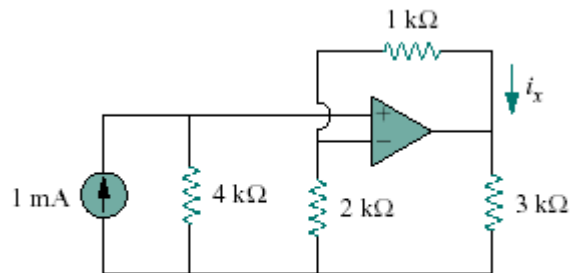


Figure 5.71  
For Prob. 5.33.