

Chapter 6, Problem 5.

The voltage across a $10\text{-}\mu\text{F}$ capacitor is shown in Fig. 6.45. Find the current waveform.

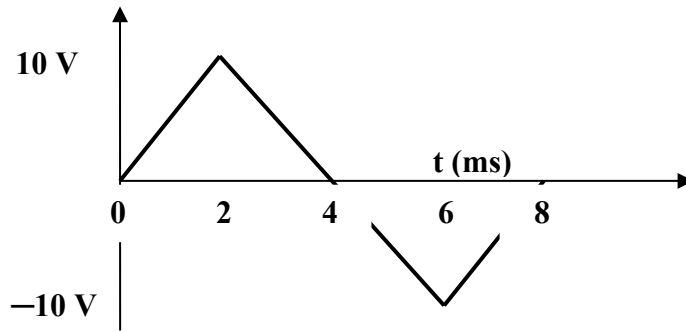


Figure 6.45
For Prob. 6.5.