

Chapter 9, Problem 74.

Design an RL circuit to provide a 90° leading phase shift.