

Chapter 9, Problem 47.

In the circuit shown in Fig. 9.54, determine the value of $i_s(t)$.

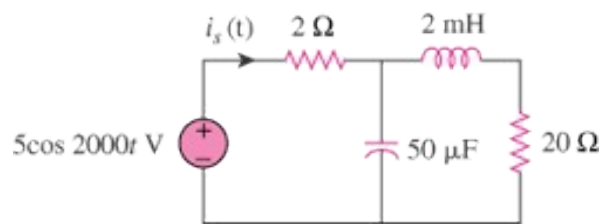


Figure 9.54
For Prob. 9.47.