

Chapter 9, Problem 57.

At $\omega = 1$ rad/s, obtain the input admittance of the circuit in Fig. 9.64.

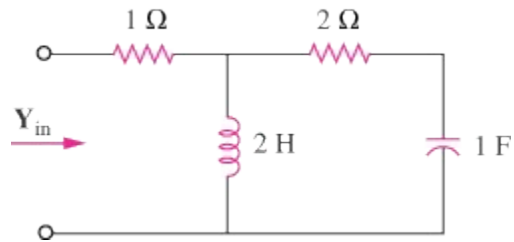


Figure 9.64
For Prob. 9.57.