

Chapter 6, Problem 81.

Design an analog computer to simulate the following equation:

$$(d^2v/dt^2) + 5v = -2f(t)$$