

**Chapter 10, Problem 1.**

Determine  $i$  in the circuit of Fig. 10.50.

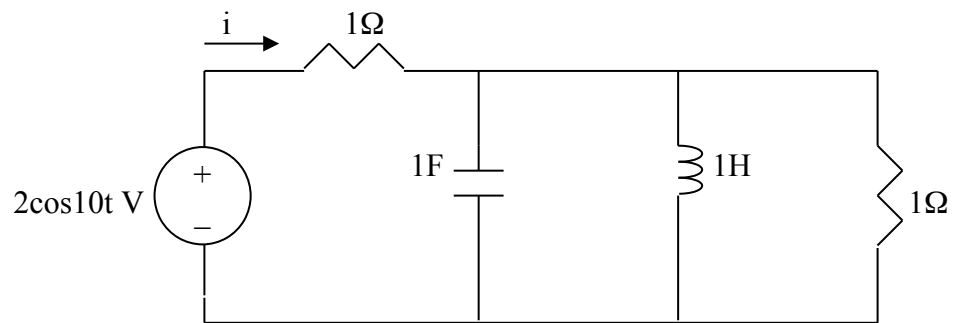


Figure 10.50  
For Prob. 10.1.