

Chapter 5, Problem 28

Find i_o in the op amp circuit of Fig. 5.66.

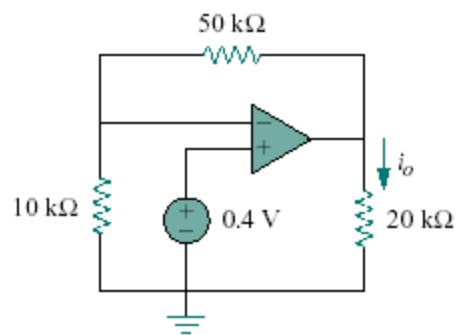


Figure 5.66
For Prob. 5.28.