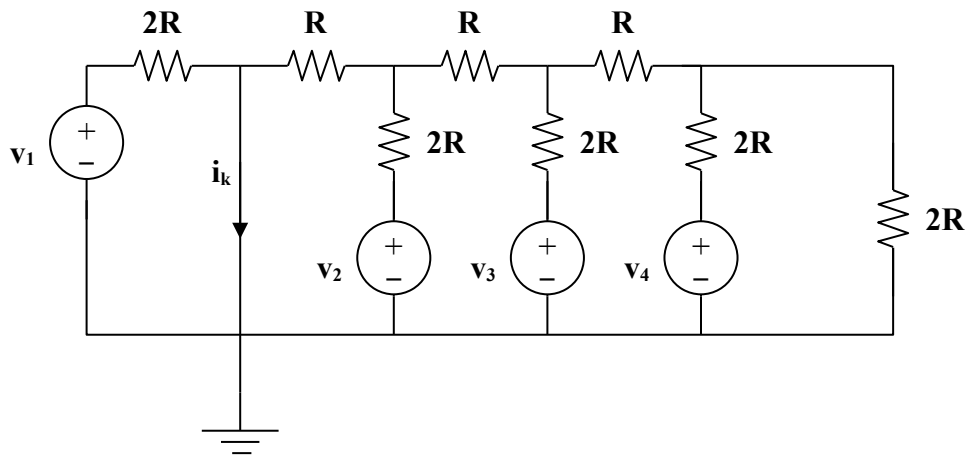


Chapter 5, Solution 84.


- (a) The easiest way to solve this problem is to use superposition and to solve for each term letting all of the corresponding voltages be equal to zero. Also, starting with each current contribution (i_k) equal to one amp and working backwards is easiest.




For the first case, let $v_2 = v_3 = v_4 = 0$, and $i_1 = 1\text{A}$.

Therefore, $v_1 = 2R$ volts or $i_1 = v_1/(2R)$.

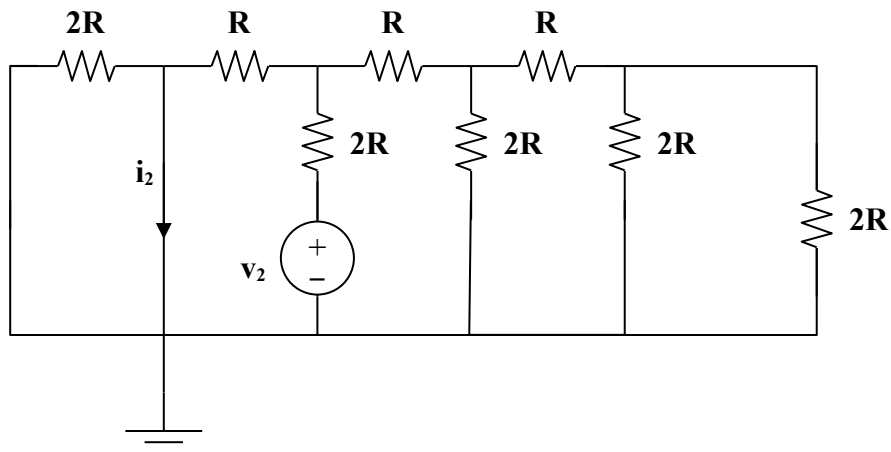Second case, let $v_1 = v_3 = v_4 = 0$, and $i_2 = 1\text{A}$.




Simplifying, we get,

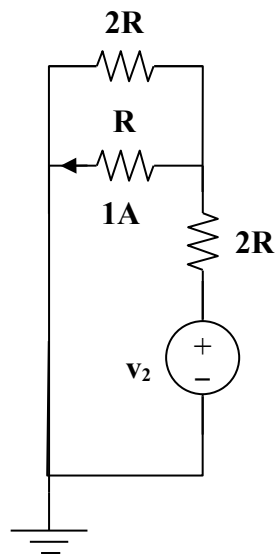

Therefore, $v_2 = 1 \times R + (3/2)(2R) = 4R$ volts or $i_2 = v_2/(4R)$ or $i_2 = 0.25v_2/R$. Clearly this is equal to the desired $1/4^{\text{th}}$.


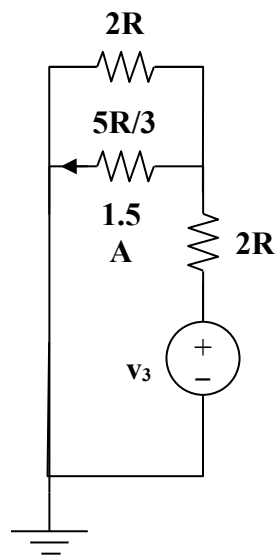
Now for the third case, let $v_1 = v_2 = v_4 = 0$, and $i_3 = 1A$.




The voltage across the $5R/3$ -ohm resistor is $5R/2$ volts. The current through the $2R$ resistor at the top is equal to $(5/4)A$ and the current through the $2R$ -ohm resistor in series with the source is $(3/2) + (5/4) = (11/4)A$. Thus,

$v_3 = (11/2)R + (5/2)R = (16/2)R = 8R$ volts or $i_3 = v_3/(8R)$ or $0.125v_3/R$. Again, we have the desired result.

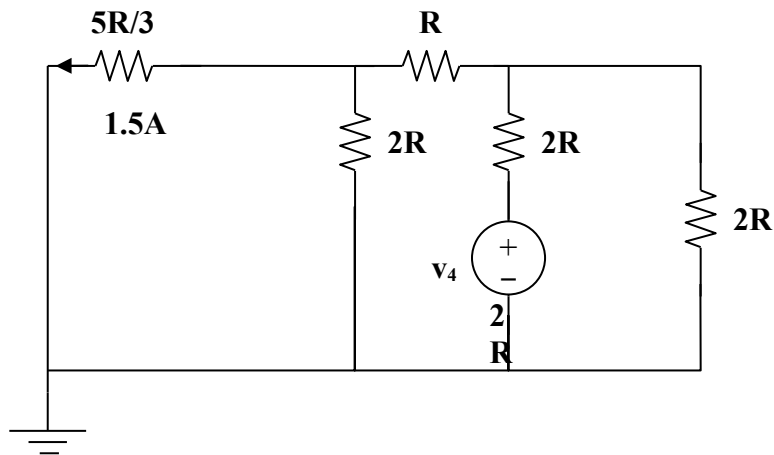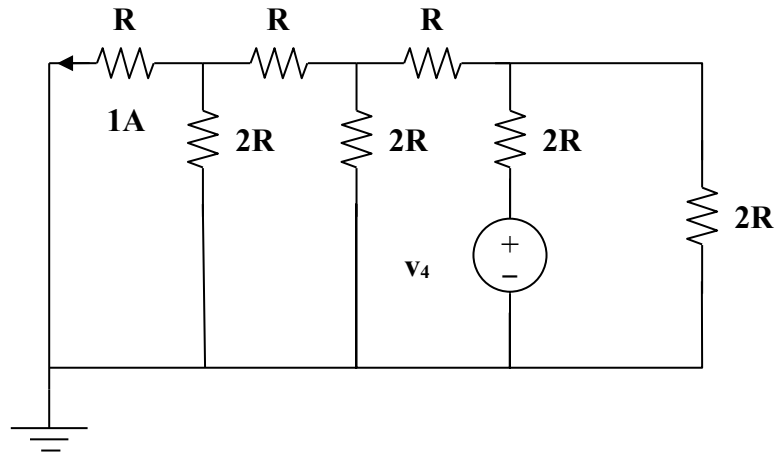For the last case, $v_1 = v_2 = v_3$ and $i_4 = 1A$. Simplifying the circuit we get,



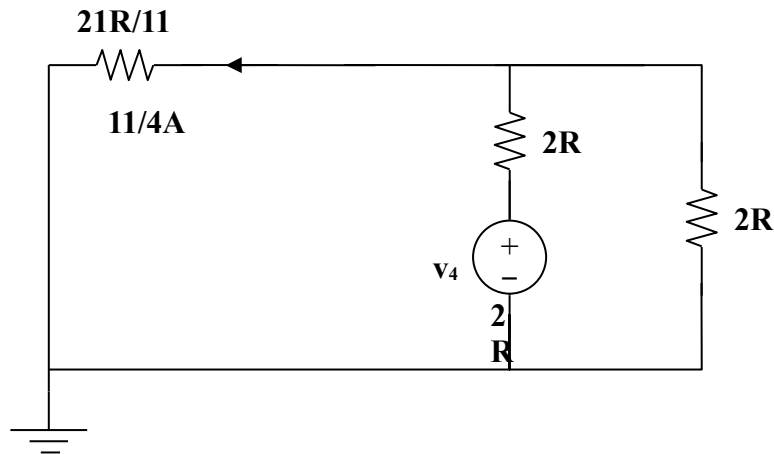

Since the current through the equivalent $21R/11$ -ohm resistor is $(11/4)$ amps, the voltage across the $2R$ -ohm resistor on the right is $(21/4)R$ volts. This means the current going through the $2R$ -ohm resistor is $(21/8)A$. Finally, the current going through the $2R$ resistor in series with the source is $((11/4)+(21/8)) = (43/8)A$.

Now, $v_4 = (21/4)R + (86/8)R = (128/8)R = 16R$ volts or $i_4 = v_4/(16R)$ or $0.0625v_4/R$. This is just what we wanted.

(b) If $R_f = 12\text{ k ohms}$ and $R = 10\text{ k ohms}$,

$$\begin{aligned} -v_o &= (12/20)[v_1 + (v_2/2) + (v_3/4) + (v_4/8)] \\ &= 0.6[v_1 + 0.5v_2 + 0.25v_3 + 0.125v_4] \end{aligned}$$

For $[v_1 \ v_2 \ v_3 \ v_4] = [1 \ 0 \ 11]$,

$$|v_o| = 0.6[1 + 0.25 + 0.125] = \mathbf{825\text{ mV}}$$

For $[v_1 \ v_2 \ v_3 \ v_4] = [0 \ 1 \ 0 \ 1]$,

$$|v_o| = 0.6[0.5 + 0.125] = \mathbf{375\text{ mV}}$$