

**Chapter 6, Solution 70.**

Using a single op amp, a capacitor, and resistors of  $100\text{ k}\Omega$  or less, design a circuit to implement

$$v_o = -50 \int_0^t v_i(t) dt$$

Assume  $v_o = 0$  at  $t = 0$ .

**Solution**

One possibility is as follows:

$$\frac{1}{RC} = 50$$

Let  $R = 100\text{ k}\Omega$ ,  $C = \frac{1}{50 \times 100 \times 10^3} = 0.2\text{ }\mu\text{F}$