

Chapter 7, Problem 47.

Determine $v(t)$ for $t > 0$ in the circuit in Fig. 7.114 if $v(0) = 0$.

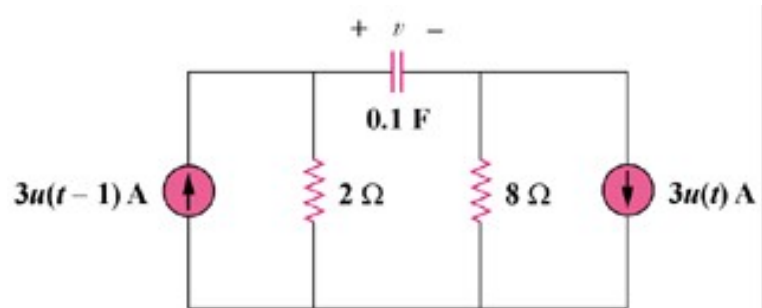


Figure 7.114
For Prob. 7.47.