

**Chapter 7, Problem 11.**

For the circuit in Fig. 7.91, find  $i_o$  for  $t > 0$ .

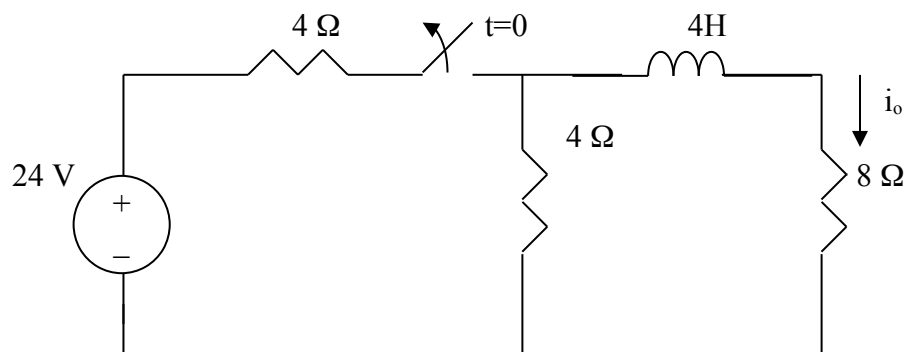


Figure 7.91  
For Prob. 7.11.