

**Chapter 6, Problem 20.**

Find the equivalent capacitance at terminals a-b of the circuit in Fig. 6.54.

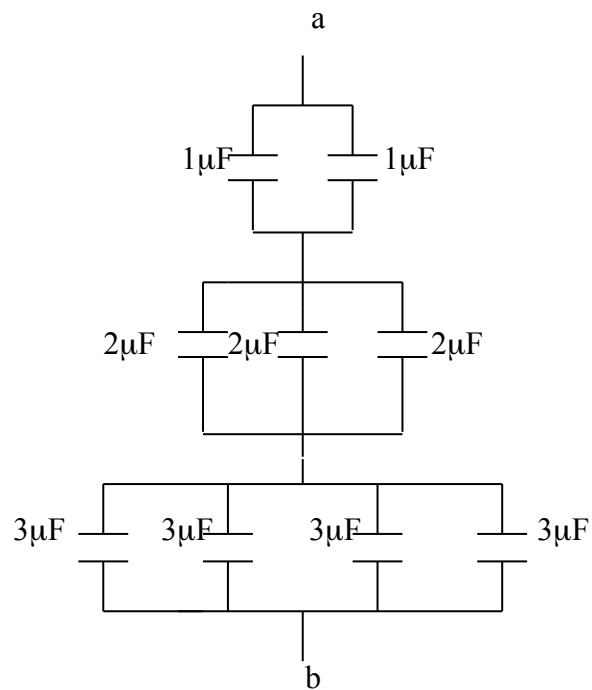


Figure 6.54  
For Prob. 6.20.