

Chapter 6, Problem 70.

Using a single op amp, a capacitor, and resistors of $100\text{ k}\Omega$ or less, design a circuit to implement

$$v_o = -50 \int_0^t v_i(t) dt$$

Assume $v_o = 0$ at $t = 0$.