

### Chapter 5, Problem 71

Determine  $v_o$  in the op amp circuit in Fig. 5.97.

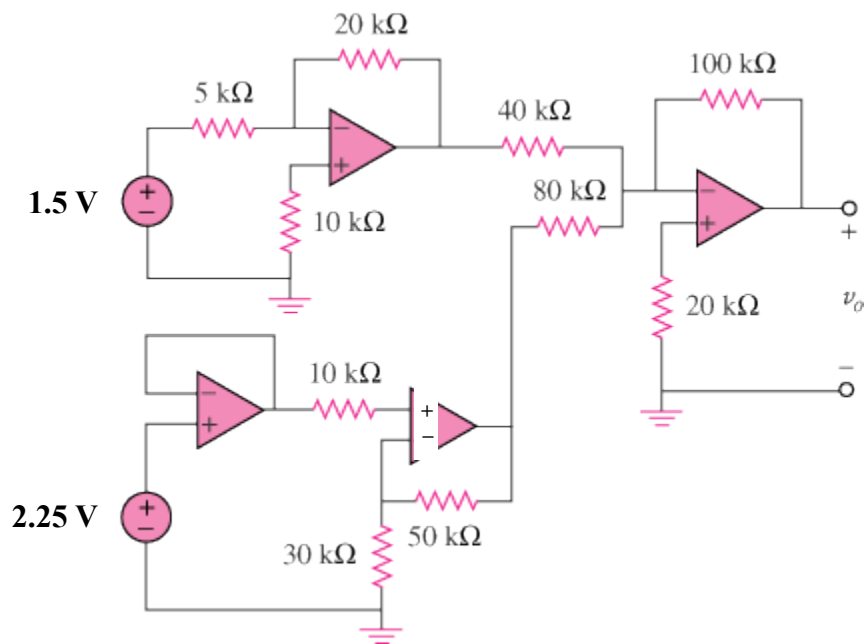


Figure 5.97  
For Prob. 5.71.