

Chapter 9, Problem 39.

For the circuit shown in Fig. 9.46, find Z_{eq} and use that to find current I . Let $\omega=10$ rad/s.

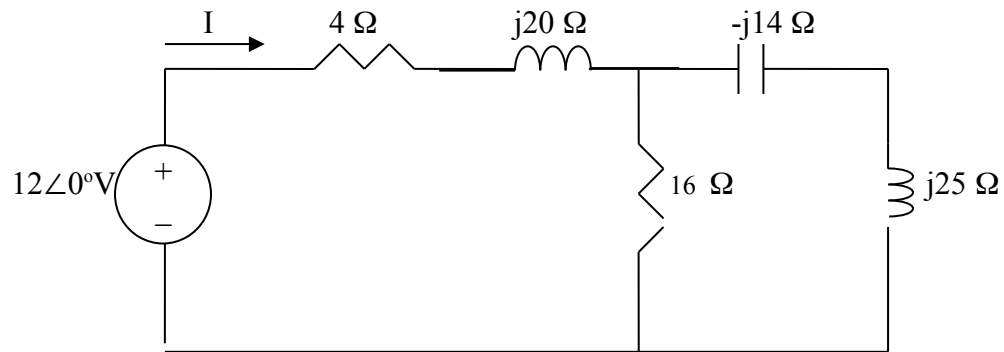


Figure 9.46
For Prob. 9.39.