

Chapter 10, Solution 60.

Find the Thevenin equivalent of the circuit in Fig. 10.103 as seen from:

- (a) terminals a - b
- (b) terminals c - d


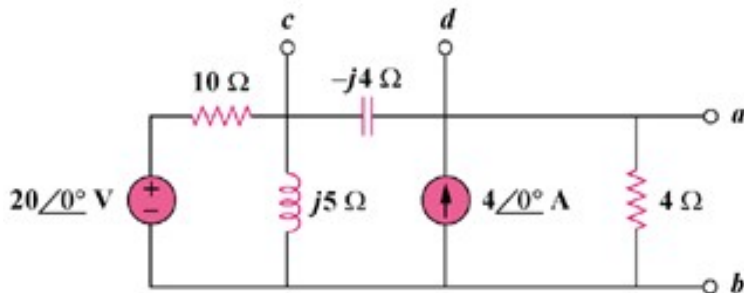


Figure 10.103
For Prob. 10.60.


Solution

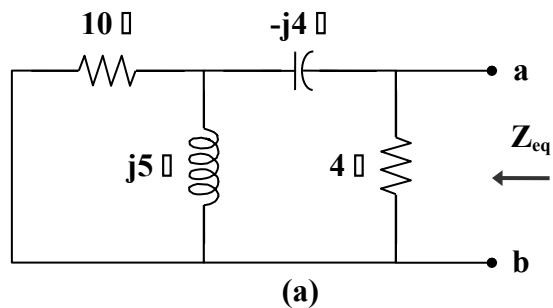

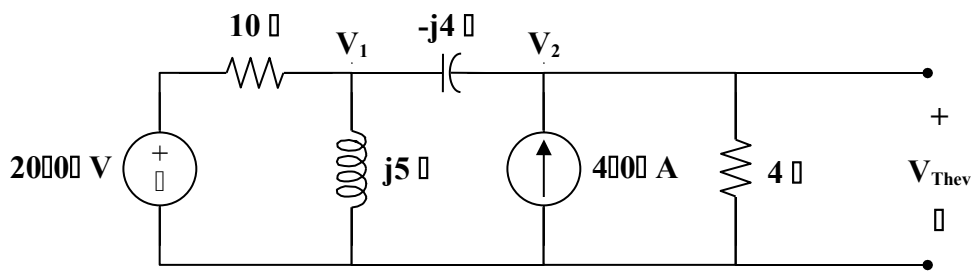- (a) To find Z_{eq} , consider the circuit in Fig. (a).

$$\begin{aligned} Z_{eq} &= 4 \parallel (-j4 + 10 \parallel j5) = 4 \parallel (-j4 + 2 + j4) \\ Z_{eq} &= 4 \parallel 2 \\ &= 1.333 \Omega \end{aligned}$$

To find V_{Th} , consider the circuit in Fig. (b).



At node 1,

$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{j5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4}$$

$$(1 + j0.5) \mathbf{V}_1 - j2.5 \mathbf{V}_2 = 20 \quad (1)$$

At node 2,

$$4 + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4} = \frac{\mathbf{V}_2}{4}$$

$$\mathbf{V}_1 = (1 - j) \mathbf{V}_2 + j16 \quad (2)$$


Substituting (2) into (1) leads to

$$28 - j16 = (1.5 - j3) \mathbf{V}_2$$

$$\mathbf{V}_2 = \frac{28 - j16}{1.5 - j3} = 8 + j5.333$$

Therefore,
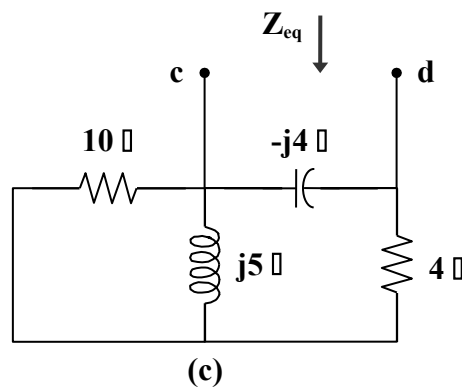
$$\mathbf{V}_{Thev} = \mathbf{V}_2 = \underline{\underline{9.615 \angle 33.69^\circ \text{ V}}}$$



- (b) To find \mathbf{Z}_{eq} , consider the circuit in Fig. (c).

$$\mathbf{Z}_{eq} = -j4 \parallel (4 + 10 \parallel j5) = -j4 \parallel \left(4 + \frac{j10}{2 + j} \right)$$

$$\mathbf{Z}_{eq} = -j4 \parallel (6 + j4) = \frac{-j4}{6} (6 + j4) = \mathbf{(2.667 - j4) \Omega}$$

To find \mathbf{V}_{Thev} , we will make use of the result in part (a).

$$\mathbf{V}_2 = 8 + j5.333 = (8/3)(3 + j2)$$

$$\mathbf{V}_1 = (1 - j)\mathbf{V}_2 + j16 = j16 + (8/3)(5 - j)$$

$$\mathbf{V}_{Thev} = \mathbf{V}_1 - \mathbf{V}_2 = 16/3 + j8 = \mathbf{9.614 \angle 56.31^\circ V}$$