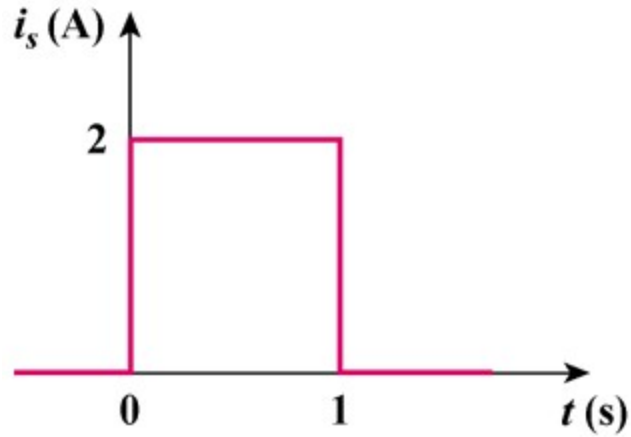


Chapter 7, Problem 76.


Repeat Prob. 7.40 using *PSpice*.

Chapter 7, Problem 49.

If the waveform in Fig. 7.116(a) is applied to the circuit of Fig. 7.116(b), find $v(t)$. Assume $v(0) = 0$.



(a)

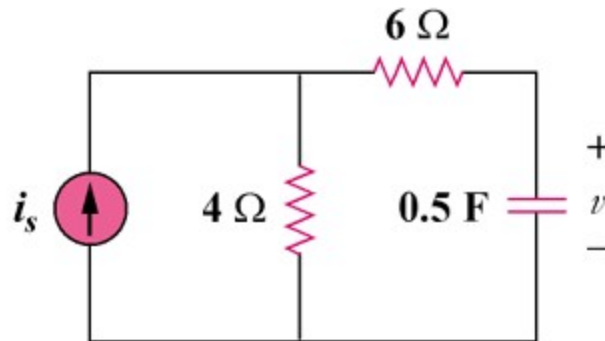

(b)

Figure 7.116
For Prob. 7.76.