

### Chapter 10, Solution 79.

For the op amp circuit in Fig. 10.122, obtain  $v_o(t)$ .


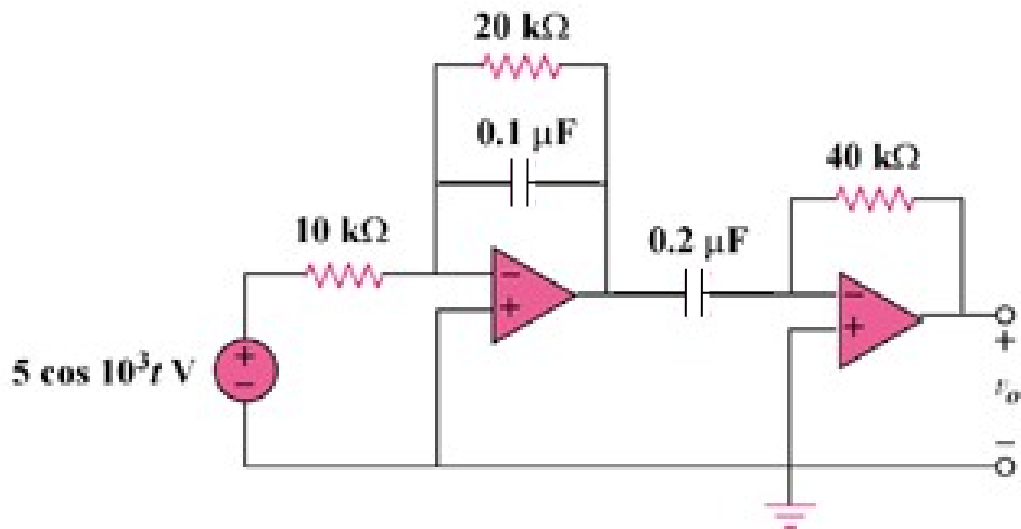


Figure 10.122  
For Prob. 10.79.

### Solution

$0.5 \cos(1000t)$	$\longrightarrow$	$0.5 \angle 0^\circ, \quad \omega = 1000$
$0.1 \mu\text{F}$	$\longrightarrow$	$\frac{1}{j\omega C} = \frac{1}{j(1000)(0.1 \times 10^{-6})} = -j10 \text{ k}\Omega$
$0.2 \mu\text{F}$	$\longrightarrow$	$\frac{1}{j\omega C} = \frac{1}{j(1000)(0.2 \times 10^{-6})} = -j5 \text{ k}\Omega$

Consider the circuit shown below.

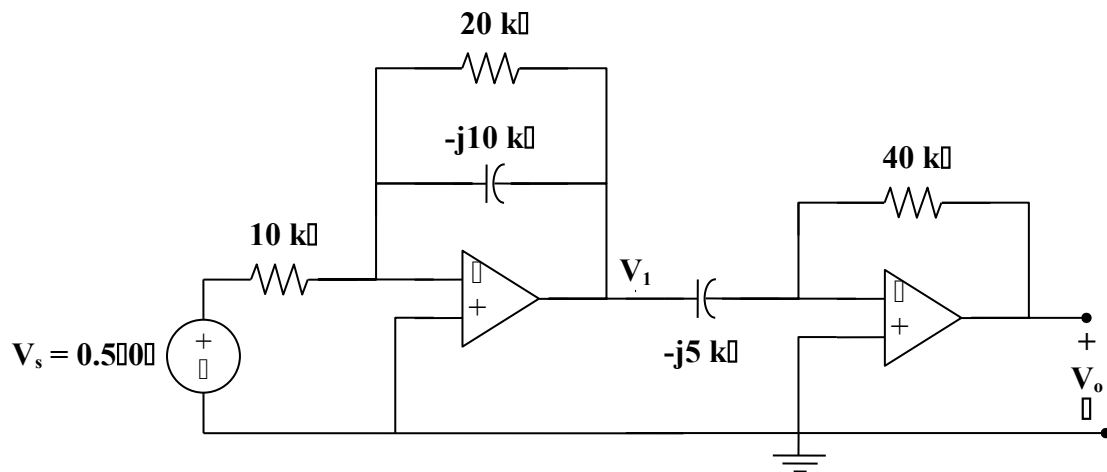

Since each stage is an inverter, we apply  $\boxed{\mathbf{V}_o = \frac{-\mathbf{Z}_f}{\mathbf{Z}_i} \mathbf{V}_i}$  to each stage.

$$\boxed{\mathbf{V}_o = \frac{-40}{-j5} \mathbf{V}_1} \quad (1)$$

and

$$\boxed{\mathbf{V}_1 = \frac{-20 \parallel (-j10)}{10} \mathbf{V}_s} \quad (2)$$

From (1) and (2),

$$\boxed{\mathbf{V}_o = \left( \frac{-j8}{10} \right) \left( \frac{-(20)(-j10)}{20 - j10} \right) 0.5 \angle 0^\circ}$$

$$\boxed{\mathbf{V}_o = 1.6(2 + j) = 35.78 \angle 26.56^\circ}$$

Therefore,  $\boxed{v_o(t) =}$  **3.578cos(1000t + 26.56°) V**