

Chapter 5, Problem 54.

Determine the voltage transfer ratio v_o/v_s in the op amp circuit of Fig. 5.82, where $R = 10\text{ k}\Omega$.

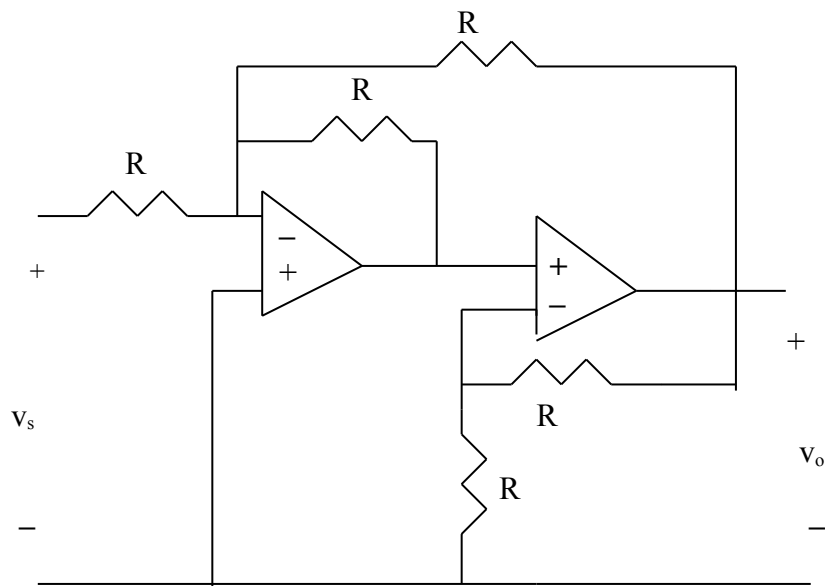


Figure 5.82
For Prob. 5.54.