

### Chapter 7, Problem 41.

Using Fig. 7.108, design a problem to help other students better understand the step response of an RC circuit.

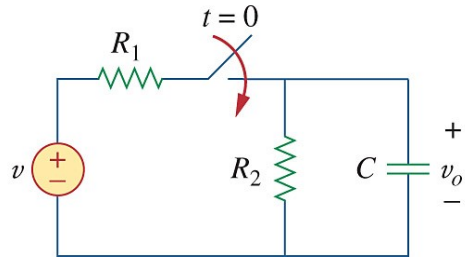


Figure 7.108  
For Prob. 7.41.