

**Chapter 6, Problem 15.**

Two capacitors ( $25\ \mu\text{F}$  and  $75\ \mu\text{F}$ ) are connected to a  $100\text{-V}$  source. Find the energy stored in each capacitor if they are connected in:

(a) parallel

(b) series