

**Chapter 7, Problem 84.**

The resistance of a 160-mH coil is  $8\Omega$ . Find the time required for the current to build up to 60% of its final value when voltage is applied to the coil.