

### Chapter 6, Solution 81

Design an analog computer to simulate the following equation:

$$(d^2v/dt^2) + 5v = -2f(t)$$

#### Solution

We can write the equation as

$$\frac{d^2v}{dt^2} = -5v - 2f(t)$$

which is implemented by the circuit below.

