

**Chapter 9, Problem 66.**

For the circuit in Fig. 9.73, calculate  $Z_T$  and  $V_{ab}$ .

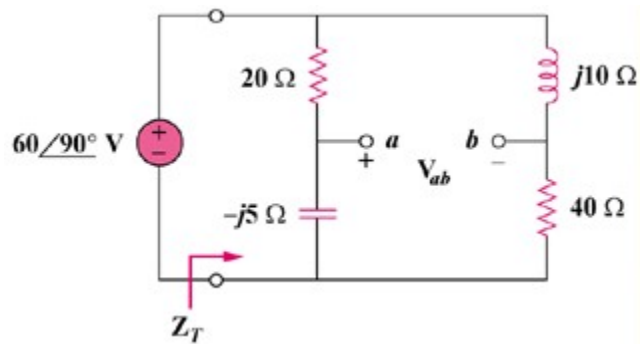


Figure 9.73  
For Prob. 9.66.