

Chapter 11, Problem 83.

Oscilloscope measurements indicate that the peak voltage across a load and the peak current through it are respectively $210\angle 60^\circ$ V and $8\angle 25^\circ$ A. Determine: (a) the real power, (b) the apparent power, (c) the reactive power, (d) the power factor.