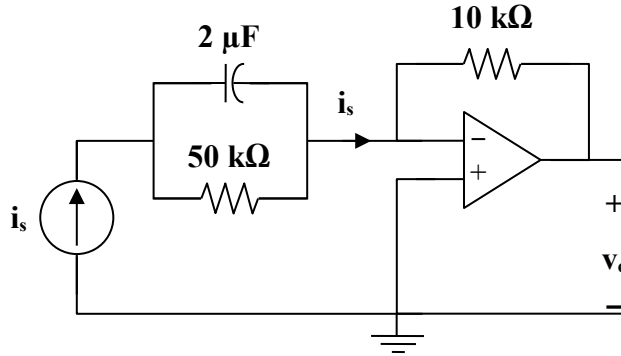


### Chapter 7, Solution 74.

Let  $v$  = capacitor voltage. For  $t < 0$ ,  $v(0) = 0$

For  $t > 0$ ,  $i_s = 10 \mu\text{A}$ .



Since the current through the feedback resistor is  $i_s$ , then

$$v_o = -i_s \times 10^4 \text{ volts} = -10^{-5} \times 10^4 = -100 \text{ mV}.$$

It is interesting to look at the capacitor voltage.

$$i_s = C \frac{dv}{dt} + \frac{v}{R}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

It is evident that

$$\tau = RC = (2 \times 10^{-6})(50 \times 10^3) = 0.1$$

At steady state, the capacitor acts like an open circuit so that  $i_s$  passes through  $R$ . Hence,

$$v(\infty) = i_s R = (10 \times 10^{-6})(50 \times 10^3) = 0.5 \text{ V}$$

Then the voltage across the capacitor is,

$$v(t) = 500(1 - e^{-10t}) \text{ mV}.$$