Chapter 11, Problem 9.

For the op amp circuit in Fig. 11.41, \mathbf{V}_s = $10 \angle 30^{\circ}$ V. Find the average power absorbed by the 20-k Ω resistor.

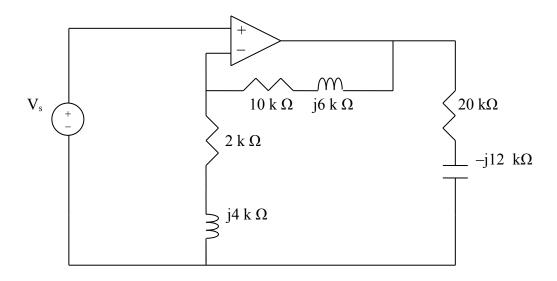


Figure 11.41 For Prob. 11.9.