

Chapter 6, Problem 2.

A 50- μF capacitor has energy $w(t) = 10\cos^2(377t)$ J. Determine the current through the capacitor.