

**Chapter 5, Problem 86**

Design a voltage controlled ideal current source (within the operating limits of the op amp) where the output current is equal to  $200v_s(t)$   $\mu\text{A}$ .