

Chapter 10, Problem 89.

The op amp circuit in Fig. 10.131 is called an *inductance simulator*. Show that the input impedance is given by,

$$\mathbf{Z}_{\text{in}} = \mathbf{V}_{\text{in}}/\mathbf{I}_{\text{in}} = j\omega L_{\text{eq}}$$

where

$$L_{\text{eq}} = [(R_1 R_3 R_4)/R_2]C.$$

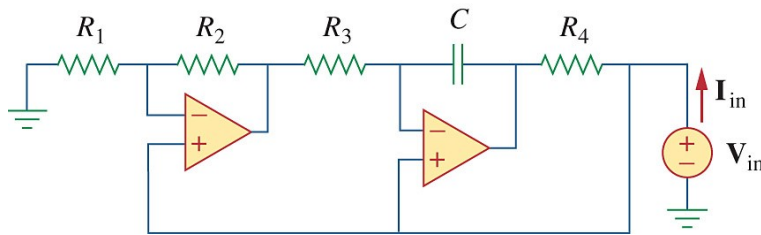


Figure 10.131
For Prob. 10.89.