

**Chapter 10, Problem 88.**

Use *PSpice* to find  $v_o$  and  $i_o$  in the circuit of Fig. 10.130.

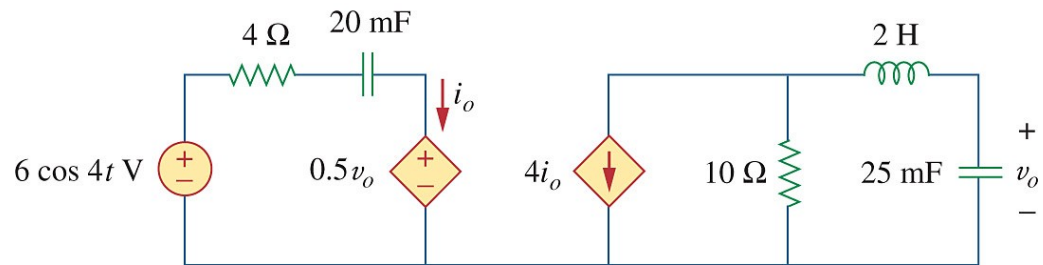


Figure 10.130  
For Prob. 10.88.