

Chapter 6, Solution 49.

Find the equivalent inductance of the circuit in Fig. 6.72. Assume all inductors are 10 mH.


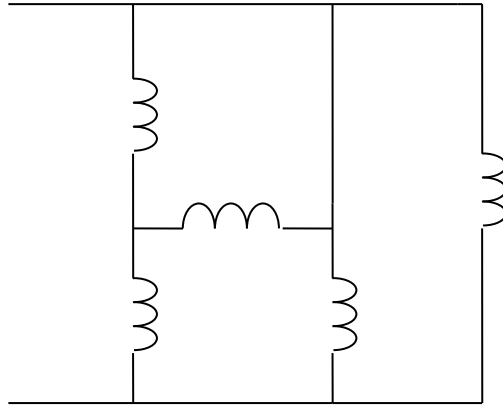


Figure 6.72
For Prob. 6.49.

Solution

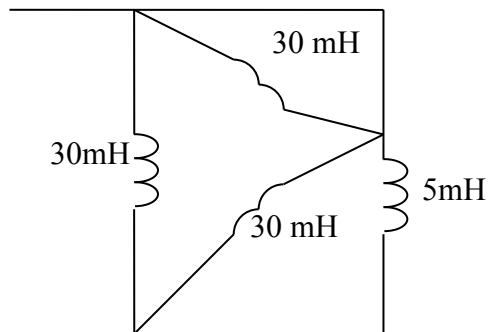Converting the wye-subnetwork to its equivalent delta gives the circuit below.



$$30//0 = 0, \quad 30//5 = 30 \times 5 / 35 = 4.286$$

$$L_{eq} = 30 // 4.286 = \frac{30 \times 4.286}{34.286} = \underline{3.75 \text{ mH}}$$