

**Chapter 10, Problem 44.**

Use superposition principle to obtain  $v_x$  in the circuit of Fig. 10.89. Let  $v_s = 50 \sin 2t$  V and  $i_s = 12 \cos(6t + 10^\circ)$  A.

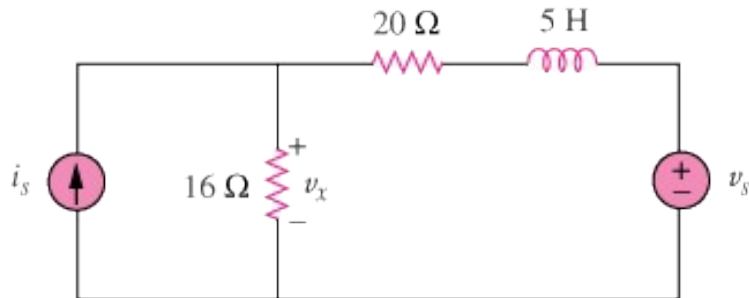


Figure 10.89  
For Prob. 10.44.