

Chapter 5, Problem 51

Using two op amps, design a subtractor.