

Chapter 11, Problem 61.

Given the circuit in Fig. 11.80, find \mathbf{I}_o and the overall complex power supplied.

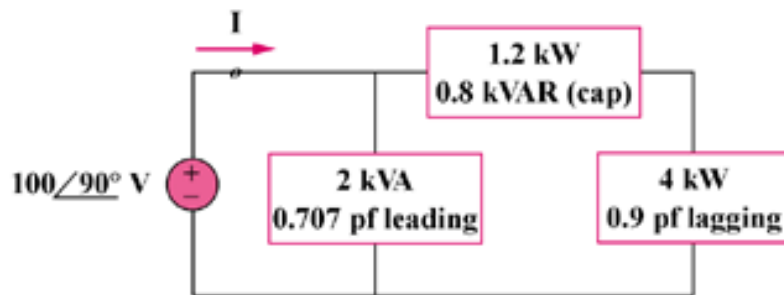


Figure 11.80
For Prob. 11.61.