

Chapter 10, Problem 83.

Use PSpice to find $v_o(t)$ in the circuit if Fig. 10.125. Let $i_s = 2\cos(10^3t)$ A.

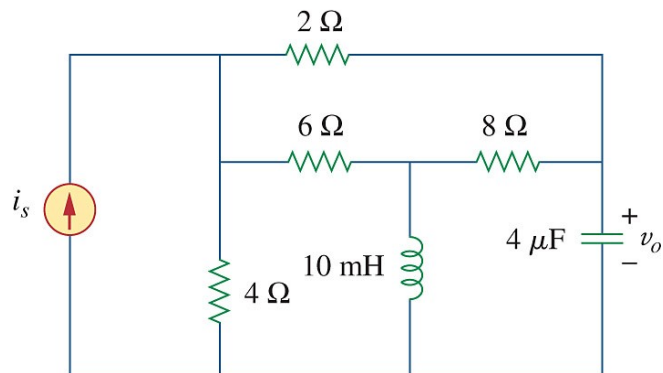


Figure 10.125
For Prob. 10.83.