

### Chapter 5, Problem 78

Use *PSpice* to obtain  $v_o$  in the circuit of Fig. 5.101.

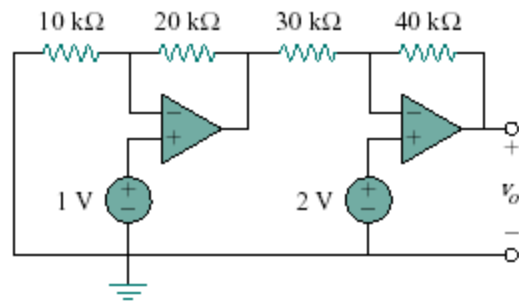


Figure 5.101  
For Prob. 5.78.