

### Chapter 5, Solution 52

Design an op amp circuit such that

$$v_o = 4v_1 + 6v_2 - 3v_3 - 5v_4$$

Let all the resistors be in the range of 20 to 200 k $\Omega$ .

#### Solution

A summing amplifier shown below will achieve the objective. An inverter is inserted to invert  $v_2$ . Since the smallest resistance must be at least 20 k $\Omega$ , then let  $R/6 = 20\text{k}\Omega$  therefore let  $R = 120\text{ k}\Omega$ .

