

Chapter 6, Problem 82.

Design an an op amp circuit such that:

$$v_o = 10v_s + 2\int v_s dt$$

where v_s and v_o are the input voltage and output voltage respectively.