
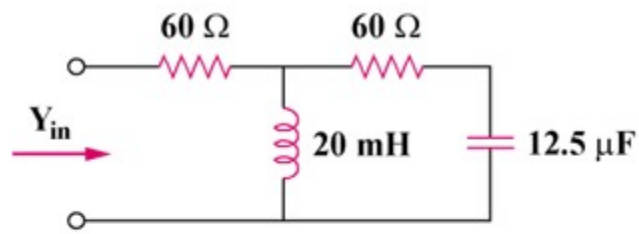


Chapter 9, Problem 67.

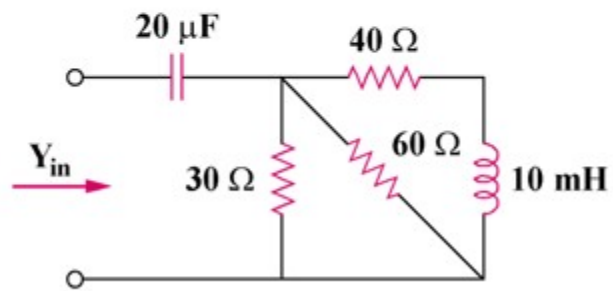At $\Omega = 10^3$ rad/s, find the input admittance of each of the circuits in Fig. 9.74.



(a)



(b)

Figure 9.74
For Prob. 9.67.