

### Chapter 6, Problem 6.

The voltage waveform in Fig. 6.46 is applied across a  $55\text{-}\mu\text{F}$  capacitor. Draw the current waveform through it.

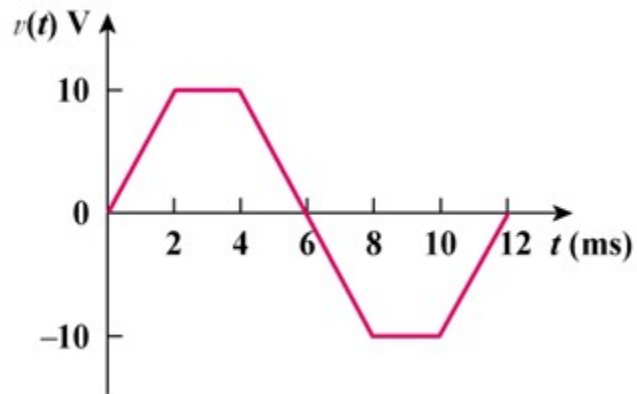


Figure 6.46  
For Prob. 6.6.