

Chapter 10, Problem 60.

Find the Thevenin equivalent of the circuit in Fig. 10.103 as seen from:

- (a) terminals a - b
- (b) terminals c - d

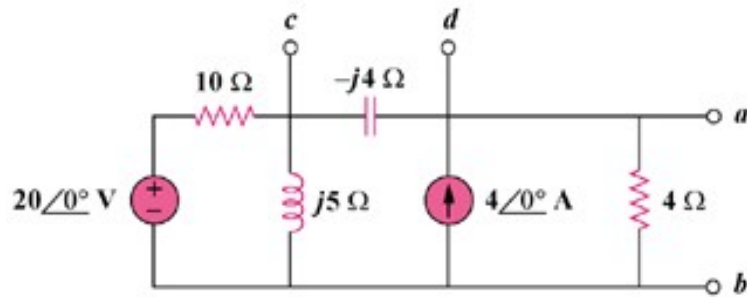


Figure 10.103
For Prob. 10.60.