

### Chapter 5, Solution 75.

The schematic is shown below. Pseudo-components VIEWPOINT and IPROBE are involved as shown to measure  $v_o$  and  $i$  respectively. Once the circuit is saved, we click Analysis | Simulate. The values of  $v$  and  $i$  are displayed on the pseudo-components as:

$$i = 200 \mu\text{A}$$

$$(v_o/v_s) = -4/2 = -2$$

The results are slightly different than those obtained in Example 5.11.

