

**Chapter 6, Problem 18.**

Find  $C_{eq}$  in the circuit of Fig. 6.52 if all capacitors are  $4\ \mu\text{F}$

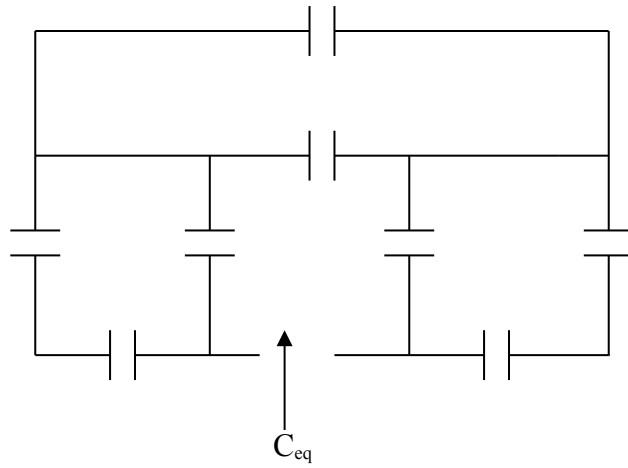


Figure 6.52  
For Prob. 6.18.