

Chapter 5, Solution 25.

Calculate v_o in the op amp circuit of Fig. 5.63.

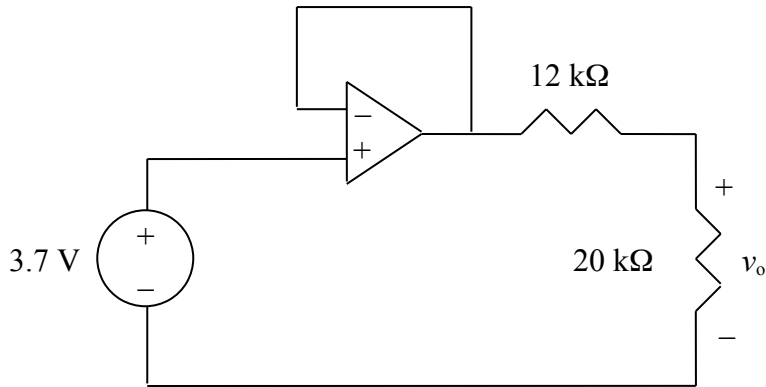


Figure 5.63
For Prob. 5.25.

Solution

This is a voltage follower. If v_1 is the output of the op amp,

$$v_1 = 3.7 \text{ V}$$

$$v_o = [20\text{k}/(20\text{k}+12\text{k})]v_1 = [20/32]3.7 = \mathbf{2.312 \text{ V}}.$$