

Chapter 10, Problem 27.

Using mesh analysis, find \mathbf{I}_1 and \mathbf{I}_2 in the circuit of Fig. 10.75.

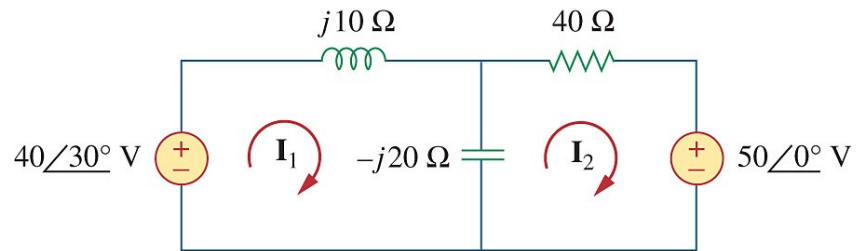


Figure 10.75
For Prob. 10.27.